

DSM Lab Report

Name: Anirudh Kaushik

Roll No: 2020111015

Group Number: 5

Objective:

1. To make an LED blink using Arduino
2. To turn on and turn off an LED using Arduino
3. To get familiarized with Arduino and Tinkercad simulation software

Experiment setup/ procedure:

Materials required:

1. 1xLED
2. 1xArduino uno
3. 5xconnecting wires
4. 1xBreadBoard
5. 1x1k Ω resistor

Procedure:

1. Take the BreadBoard and connect an LED across row b holes 14(Cathode) and 15(Anode).
2. Connect a wire(red) in row a hole 14 to the second last row marked (-) in the hole in the same column.
3. Connect a wire(red) in the adjacent hole in the second last row marked (-) to the port marked GND(ground) in the Arduino.
4. Connect the 1k Ω resistor in row c in holes 19 to 23.
5. Connect a wire(green) in row d from holes 15 to 19 such that the wire in the hole just above the resistor.
6. Connect a wire(black) in row d hole 23 (right above the resistor) to the hole in the corresponding column in the second row from the top marked(+).
7. Connect a wire(black) in the column corresponding to hole 25 in the second row from the top marked(+) and connect its other end to the Arduino port marked 13.
8. The connections are now complete and the LED should blink when the code stated below is entered.

Code:

```
void setup()
{
  pinMode(13, OUTPUT);
}

#define ON HIGH //to substitute ON instead of HIGH
#define OFF LOW //to substitute OFF instead of LOW

void loop()
{
  digitalWrite(13, ON); //switches the LED ON
  delay(1000); // Wait for 1000 millisecond(s)
  digitalWrite(13, OFF); // switches the LED OFF
  delay(1000); // Wait for 1000 millisecond(s)
}
```


Conclusion:

1. Successfully learnt how to use basic functions of Tinkercad simulation software.
2. Successfully learnt how to use basic functions of an Arduino.
3. Successfully made an LED blink with a delay of 1000 microseconds by inputting required code in Arduino.
4. Familiarized ourself with the connections in a BreadBoard.

Tinkercad Link with Circuit:

https://www.tinkercad.com/things/anj8QAJp52u-swanky-snicket-luulia/editel?sharecode=hpATYZ_owYs6cyRfPvwWj47YV7xzaNFzFDo09Wnxh9k

Circuit Diagram:

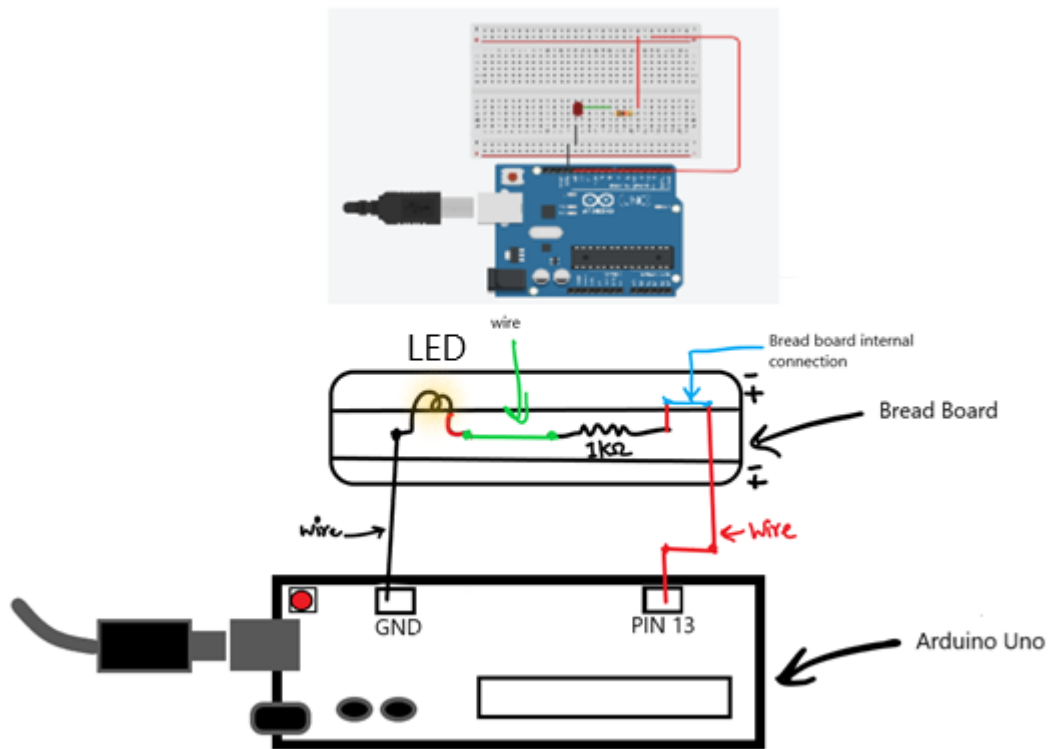

MADE USING PAINT 3d